#### Welcome to Effectrode!

• My Cart - \$0.00

### **Shopping Cart**

• Search for: Search for products Search

### **Effectrode**



- HOME
- ABOUT
- PEDALS »
- NEWS
- STORE »
- DEALERS
- ARTISTS
- SUPPORT »



Guitar Tone is Rocket Science! - Vintage, high voltage, vacuum tube technology harnessed to create exceptional effects pedals.

#### Buy Now!

Home / Blackbird Vacuum Tube Preamp / Guitar Preamp Tone Explained

## **Guitar Preamp Tone Explained**

### by **Phil Taylor**

During the research and development of the <u>'Blackbird' vacuum tube preamp</u> I undertook a thorough investigation into tube preamp circuits in a quest to discover just what factors are important in creating great guitar tone. The following article is a result of those labours . . .

The interplay between your guitar, amp and playing technique are all fundamental to your tone. Your amp responds or reacts in a certain way to the signal from your guitar pickup, the pickup responds to the way you pick the strings and in turn you react to the sound you hear coming from your amp. The whole system is a closed loop with the implication that your guitar and amp will influence your playing in a significant way – the right guitar and amp setup will let your playing soar whilst the wrong setup will hold you back, keeping you well and truely grounded. It's impossible to over-emphasise the importance of the relationship between gear and musician – it's certainly worth delving into the science a little and discovering what makes great tone. This article specifically explores tube guitar preamp circuitry – the

aim is to demystify the tube sound, give a clear explanation of what's happening within the preamp, and gain an insight into how guitar legends created their wonderful, classic guitar sounds.

### What's Inside?

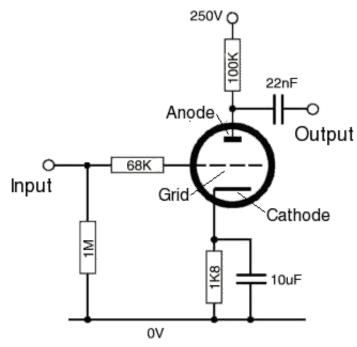


Figure 1 – Common cathode tube amplifer.

#### **Tube Distortion**

Distortion is low in this type of amplifier circuit as the 1K8 cathode resistor sets the bias point right in the middle of the tube's linear region as shown in Figure 2. Figure 2 shows the 'transfer function' or 'load line' for this amplifier. The small input voltage (x-axis) controls anode current (y-axis) flowing through the tube to give amplification. This centre biased amplifier section has the maximum threshold of clipping possible (highest headroom), that is where the grid can be fed with the largest possible signal before clipping. Another way of putting it, is to say the input sensitivity of the stage is at its lowest (input sensitivity describes the input voltage required to drive the stage into the non-linear region on the curve and cause clipping). Consequently, this is a very clean sounding amplifier and introduces relatively little distortion into the signal – early guitar amp manufacturers weren't striving to generate huge amounts of overdrive and sustain with their circuits, just amplify the signal so the

Your tube amp is made up of a preamp section and power amp section, both of these contribute to the overall tone and feel of the amp. Figure 1 on the left shows a typical tube preamp stage. This type of circuit is called a common cathode gain stage and is found in many classic Fender amps, including the early Deluxe and Twin Reverb 'Blackface' and 'Silverface' amps. This circuit is a standard building block for amplifier circuits and is used by many other manufacturers including Soldano, Boogie, Marshall and Effectrode in their effects pedals. This circuit turns a small voltage into a large voltage – it's a voltage amplifier. With a 12AX7 tube in there this circuit gives about 30dB of voltage gain, with a 12AU7 expect about 15dB of gain. In a typical vintage amp this gain stage is followed by passive tonestack and then a power stage drive section.

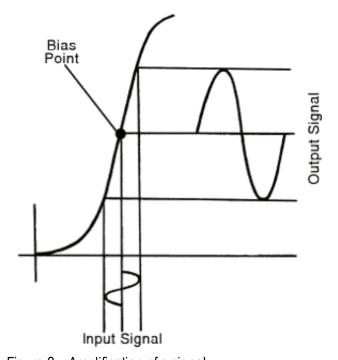


Figure 2 – Amplification of a signal.

guitar could be heard above the drums.

The non-linearity inherent in tubes means that there will always be small amounts of distortion introduced into the signal, even with a clean amp such as the *Fender Twin*. This is partly explains why a tube amp sounds warmer and has a more musical character than a solid-state amp. The sound of many great Rock 'n' Roll players such as Ritchie Valens, Buddy Holly and Chuck Berry were defined by amps with cathode follower preamp stages. Although the preamp section of these amps is relatively clean sounding, the power amp section generates significantly more signal distortion, especially when the amp is cranked up. The distortion is the result of several factors including:

- The power amp tubes entering the clipping region
- The rectifier tube voltage sagging
- The transformer core becoming saturated
- The speaker cone resonances and/or break-up

This subject, however, is outside the scope of this article – so let's get back to the preamp section.

## **Symmetrical Clipping**

This preamp section can be made to distort (in a very pleasant way) if fed with a large enough signal and that's exactly what guitarists did during the late 60s and early 70s. Players like Alex Lifeson, Jimmy Page and Robin Trower pushed their amps into distortion by placing a boost pedal before their rig (typically a wall of Hi-watt or Marshall tube heads feeding into 4 x 12 cabs!). Because the bias point of the first amp section is roughly in the middle of the load line, the guitar signal is clipped roughly equally on both sides – symmetrical clipping as shown in *Figure 3*.

Symmetrical clipping produces a mixture of odd and even order harmonics creating the classic rock distortion tone. What you're hearing when you use a boost pedal is actually your tube amp distorting – that is, a significant amount of the tonal character of the overdrive tone is generated by the amp. *Figure 4* shows a frequency analysis of a centre-biased 12AX7 being overdriven. The

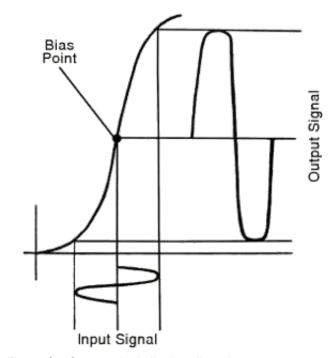


Figure 3 – Symmetrical clipping distortion.

fundamental is a 440Hz sine wave ('A') and strong 3rd, 5th, 7th, etc harmonics are clearly present in the output signal. Even harmonics are also present, however at reduced amplitude in comparison to the odd harmonics. Although centre biased symmetric clipping distortion is beginning to approach a square wave, the rounded edges ensure that brittle-sounding high order harmonics are absent. Incidentally, a true square-wave is made up of a series of only odd harmonics – this is the kind of distortion produced by hard-clipping diode circuits found in opamp based stompboxes such as the Boss DS-1.

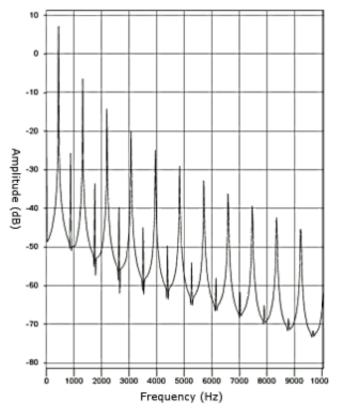


Figure 4 – Symmetrical clipping produces a signal with strong odd order harmonics.

## **Asymmetrical Clipping**

It wasn't long before designers began experimenting with multi-stage tube preamplifier circuits - pioneers of the art include Alexander Dumble, Randall Smith and Mike Soldano. Their amps contained several tube stages in series (typically four stages) to massively boost the input signal until it went outside the linear region of the tube. Additionally, by manipulating the bias point on the load line they could exercise a degree of control over the input sensitivity in each stage of the amp so that the signal clipped in a more controlled manner. Because the bias point is offset from the centre of the load line, the output signal clips to a greater extent on one half of the cycle than the other – this is asymmetric clipping. Reducing the value of the 1K8 cathode resistor causes more anode current to flow so that the tube runs physically hot. This shifts the bias point to the right-hand end of the load line and the output signal will be clipped on the positive cycle of the output signal – this is called grid current limiting

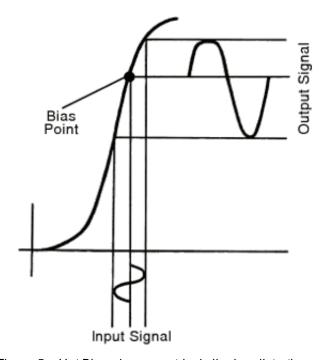


Figure 5 – Hot Biased asymmetrical clipping distortion.

and is shown in *Figure 5*. A moderate amount of hot biasing produces a smooth, warm and 'bluesy' drive, too much and the sound becomes more aggressive and 'fuzzy'

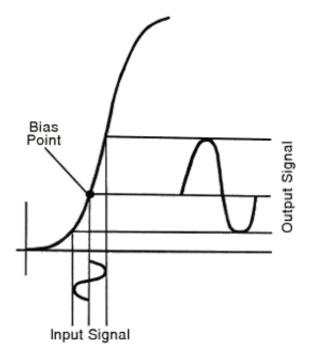


Figure 6 – Cold Biased asymmetrical clipping distortion

The bias point can also be shifted to the left-hand end of the load line by increasing the value of the cathode resistor to reduce the current flowing in the anode – this is called cold biasing. This generates cut-off clipping on the negative cycle of the output signal producing a 'crunchier', 'harderedged' distortion as shown in *Figure 6*. Cold biasing is used in many modern triode high gain tube amp designs as it adds rich, harmonic content giving a 'heavier' and 'crunchier' distortion tone.

Asymmetric clipping generates a signal rich in even and odd order harmonic overtones. The second harmonic is particularly strong (see *Figure 7* below), which is almost certainly one of the reasons tube amps sound so musical – the second harmonic is exactly one octave above the fundamental. Both symmetric and asymmetric clipping occur in a multi-stage tube preamp and it will consequently produce a tone that is a

complex mix of even and odd order harmonics. Designing an an amp is an art and involves a substantial amount of experimentation in the quest to discover the ideal biasing point, interstage tone-shaping and gain for each stage. The biasing point of each tube stage affects how the stages interact to produce distortion, ultimately defining the core tone of the amp – whether it is glassy clean, warm and bluesy, classic rock or creamy and sustaining.

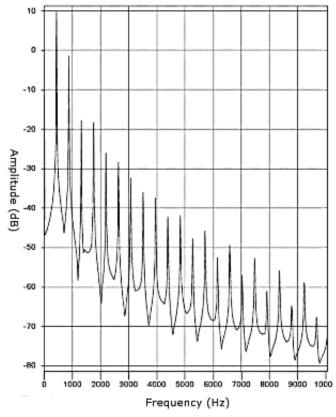


Figure 7 – Asymmetrical clipping produces a signal that is rich in even and odd order harmonics.

Demonstrations of asymmetric and symmetric tube clipping distortion can be heard on the *Blackbird* vacuum tube preamp sound clips page.


This article was also published in <u>Tone Ouest Report magazine in March 2014.</u>

### In This Section

- Manuals
- <u>Video</u>
- Sounds
- Reviews
- Customer Comments
- Supplemental
- Guitar Preamp Tone Explained
- All Flavours of Fuzz, Overdrive and Distortion
- Sample Settings
- Swapping Tubes in the Blackbird

## **News, Updates and Articles**



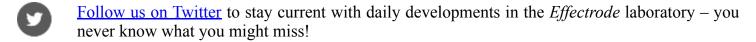

Do check out our sound clips of Effectrode pedals on SoundCloud. Full explanations are given of how each sound clip was recorded. Special thanks to all the musicians that have contributed recordings.



Well researched articles about the history and technical aspects of guitar gear and what's really important for tone – all with zero marketing hype – just the facts. This is in-depth, esoteric stuff you will not find anywhere else online, in guitar magazines and especially Wikipedia! You can find the full list of current articles here.




### Contact

**P:** +44 (0) 1782 372210 **E:** sales@effectrode.com
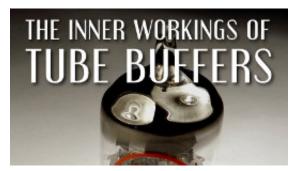
#### **Tube Buffers**

Find out just what's inside an Effectrode pedal! This article explores the deep inner workings of tube buffers, comparing and contrasting them with their solid-state transistorised opamp (operational amplifier) equivalents, and suggests why tube circuitry sounds so pleasing to the ear and musical in



comparison. Read the full article here.

# **Basic Amplifiers Film**

You may also want to take a look at this excellent US Army Training Film TF11-3419 'Basic Amplifiers' made in 1963 for more information on tube amplifier theory:

Electronics: "Basic Amplifiers" pt1-2 1963 US Army Training Film



Electronics: "Basic Amplifiers" pt1-2 1963 US Army Training Film



### **Recent Posts**



# **Effectrode in the movie industry!**

Posted on April 25, 2016

A while back Effectrode was asked if we could help out making props for the ...



# Wanted: Wrecked Echorec Drums for Scientific Research

Posted on April 18, 2016

Can anyone help? I'm looking for old, damaged or beaten-up Binson ...



# **Mercury Rising**

Posted on April 13, 2016

Well not strictly true – the Mercury fuzz is actually the only of our ...

### **Recent Comments**

- Phil: Hi Ziv, You might be able to determine the vintage of the tube from the Mul...
- ziv: Unless Mullard was no longer making the I6312AX7 by 1079.....
- **ziv**: Hello, I read different articles on your site with great interest and fi...

# Find a Dealer

Zip:	
Search	

© 2016 Effectrode.

- •
- •
- •